
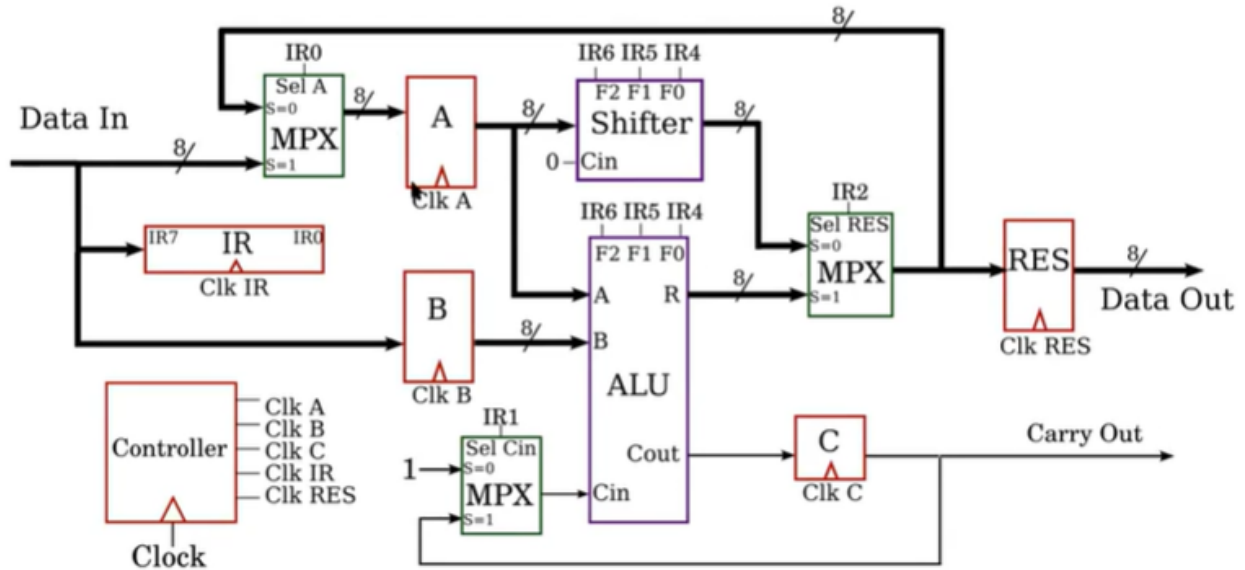


# L18 - Designing a Central Processor Unit 1 The Architecture

The Manual Processor

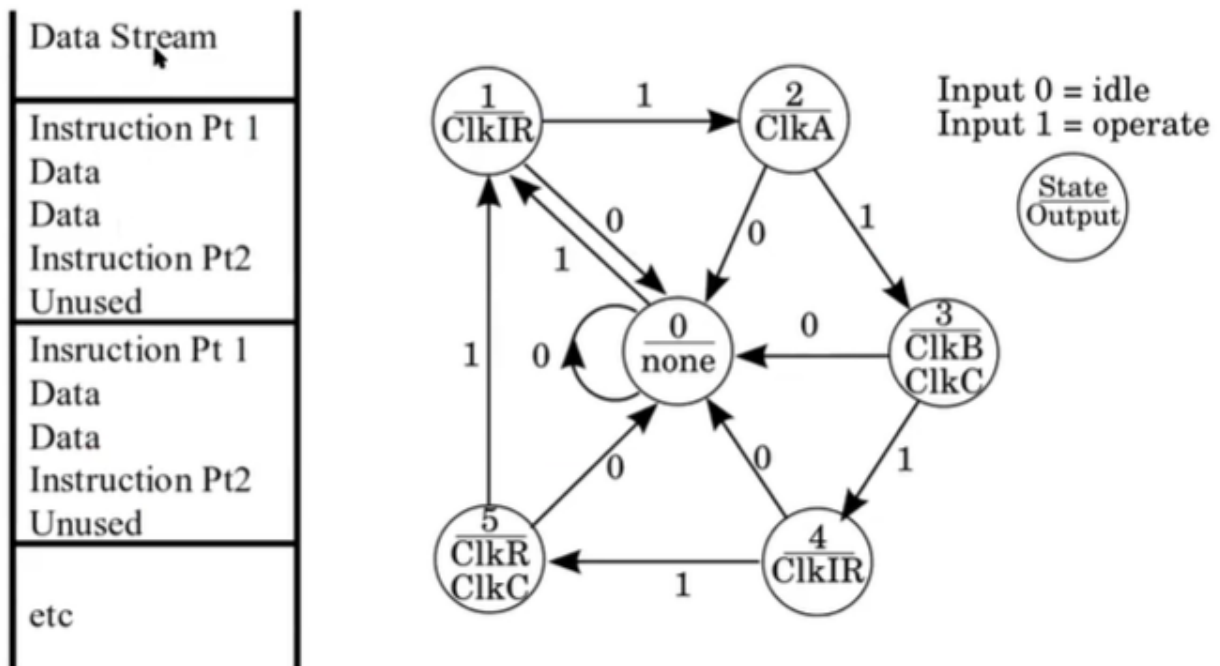


Execution Cycle



## Executing Instructions

1. Set the multiplexers so that the correct registers are connected together
2. Set the arithmetic hardware to compute the correct function
3. Provide a clock falling edge to the registers that are to change

## Fetching From Memory

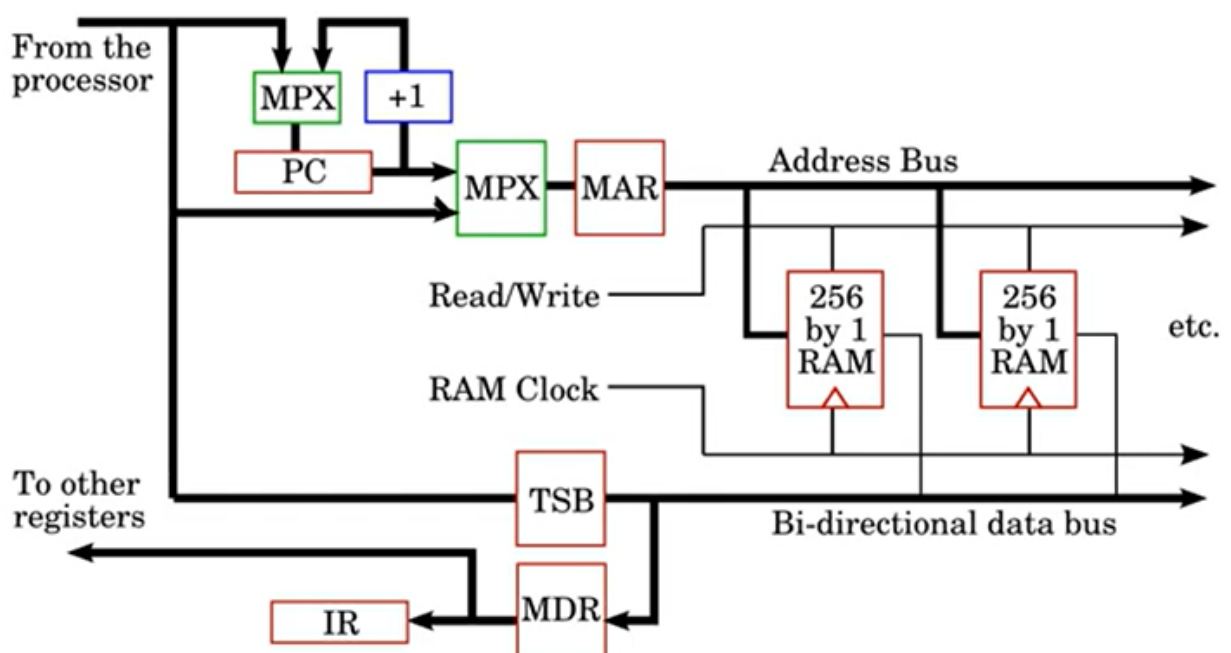






In step 2, two instructions can be executed at the same time because of how DQ flip flops work (data can be loaded into D and taken out through Q at the same time).

### Observations

1. Registers A, B, PC, MAR, MDR, IC and C belong to the hardware designers
2. Registers R0-6 can be manipulated by the programmers
3. Most arithmetic operations will no longer require a carry in, so we can set the ALU Cin directly from the controller if required (e.g. for an increment or a jump instruction)
 
### The controller Spec

The controller is going to be a sequential circuit looking something like this:



Always the same three fetch states. During the F states instructions are fetched from memory. There can be any number of Execute states, depending on the complexity of the instruction. During the E states instructions are executed.

The Fetch cycle will get one 32 bit instruction from the memory. The execute cycles will make the processor carry out that instruction. So, to formalise our spec we need to define what the instructions will do.

### The program Instructions

Assembler instructions are a compromise between the software specialists and the hardware designers.

From the software point of view, instructions should be few but very powerful.

From the hardware point of view, instructions should be simple and take only a few clock pulses to execute. A compromise must be found.

## Instruction Format

We need to be very precise about our instruction format so that we can easily interpret it in hardware. We will assume that there will be 255 or less instructions, and the top eight bits will define the instruction. Most instructions will act on a register, so we will let the next four bits define the destination register.

We have 7 registers, we only need 3 bits, why do have 4? We reserve one bit to have a little headroom to improve our processor in the next version.



## Memory Reference Instructions

There are four basic instructions that reference the memory directly:

- **LOAD Reg, Address**
- **STORE Reg, Address**
- **JUMP Address**
- **CALL Reg, Address**

LOAD Reg, Address = Load the contents at Address into Reg

STORE Reg, Address = Store the contents in Reg into address

JUMP Address = Jump to Address (overriding PC)


CALL Reg, Address = Jump to Address, then jump back to return address (stored in Reg)
 
## Function of bit mask

The memory reference instructions contain a memory address in the bottom 20 bits. The bit mask converts this unsigned 20 bit number to a 32 bit number by masking the top bits.




- **MOVE Rdest, Rscr**
- **ADD Rdest, Rscr**
- **SUBTRACT Rdest, Rscr**
- **AND Rdest, Rscr**
- **OR Rdest, Rscr**
- **XOR Rdest, Rscr**
- **COMPARE Rdest, Rscr**  
(Subtract but without storing the result)



Move: move the content of one register to another.
 
#### 1 Register Instructions

- **CLEAR Rdest**
- **INCREMENT (INC Rdest)**
- **DECREMENT (DEC Rdest)**
- **COMPLEMENT (COMP Rdest)**
- **ARITHMETIC SHIFT LEFT (ASL Rdest)**
- **ARITHMETIC SHIFT RIGHT (ASR Rdest)**
- **ROTATE RIGHT (ROR Rdest)**
- **RETURN**



Complement: Just flipping the bits, not adding one

Return: Used with a CALL instruction, returns to return address




## No Register Instructions

Following an arithmetic or compare operation:

1. SKIPPOSITIVE (skip next line if positive)
2. SKIPNEGATIVE (skip next line if negative)

Unconditional

1. SKIP
2. NOP

 

Input and Output

1. Input and output will be achieved using the LOAD and STORE instructions
2. many peripherals, disks, serial ports, etc can be read or written to as if they were memory
3. They can also be connected directly with the memory so that input and output can be done while the processor is otherwise engaged

Register transfers

1. Each of the instructions that we have specified requires a series of register transfers to carry them out
2. We continue our design, by determining the register transfers that will be needed to carry out each instruction
3. These register transfers will become the formal spec of the processor controller

Register Transfers and Processor operation

1. At each step of the execution cycle a number of register transfers take place
2. In the Fetch steps, the register transfers are always the same
3. In the execute steps the register transfers depend on the instruction being executed

## Fetch Register Transfers


The MDR is the only register connected to the memory data out bus (in the version of the processor). Three states are required to fetch an instruction:

- F1:  $MAR \leftarrow PC; PC \leftarrow PC + 1$
- F2:  $MDR \leftarrow \text{Memory}$
- F3:  $IR \leftarrow MDR$

After F3 has finished, the instruction is in both IR and MDR.


## Memory reference Instructions

Instruction	Cycle	Transfers	Path
LOAD Rdest, Address	E1	$MAR \leftarrow MDR$	Via the bit mask
	E2	$MDR \leftarrow \text{Memory}$	
	E3	$Rdest \leftarrow MDR$	No Mask
STORE Rdest, Address	E1	$MAR \leftarrow MDR; A \leftarrow Rdest$	Via the bit mask
	E2	$\text{Memory} \leftarrow A$	Shifter (unchanged)
JUMP Address	E1	$PC \leftarrow MDR$	Via the bit mask
CALL Rdest, Address	E1	$PC \leftarrow PC + 1$	
	E2	$Rdest \leftarrow PC$	
	E3	$PC \leftarrow MDR$	Via the bit mask

 

## Indirect Memory Reference Instructions


Instruction	Cycle	Transfers	Path
LOADINDIRECT Rdest, Rsrc	E1 E2 E3 E4	$A \leftarrow Rsrc$ $MAR \leftarrow A$ $MDR \leftarrow \text{Memory}$ $Rdest \leftarrow MDR$	No Mask
STOREINDIRECT Rdest, Rsrc	E1 E2 E3	$A \leftarrow Rsrc$ $MAR \leftarrow A; A \leftarrow Rdest$ $\text{Memory} \leftarrow A$	via the shifter via the shifter
JUMPINDIRECT Rsrc	E1 E2	$A \leftarrow Rsrc$ $PC \leftarrow A$	via the shifter
CALLINDIRECT Rdest, Rsrc	E1 E2 E3	$PC \leftarrow PC + 1; A \leftarrow Rsrc$ $Rdest \leftarrow PC;$ $PC \leftarrow A$	via the shifter

 

## 2 Register Instructions

Instruction	Cycle	Transfers	Path
MOVE Rdest, Rsrc	E1 E2	$A \leftarrow Rsrc$ $Rdest \leftarrow \text{Shifter}$	Shifter (unchanged)
ADD Rdest, Rsrc	E1 E2 E3	$A \leftarrow Rsrc$ $B \leftarrow Rdest$ $Rdest \leftarrow \text{ALUres};$ $C \leftarrow \text{ALUcout}$	$\text{ALU} = A + B, \text{Cin} = 0$
COMPARE Rdest, Rsrc	E1 E2 E3	$A \leftarrow Rsrc$ $B \leftarrow Rdest$ $C \leftarrow \text{ALUcout}$	$\text{ALU} = A - B, \text{Cin} = 0$

 (Plus similar arithmetic and logical operations)



## 1 Register Instructions

Instruction	Cycle	Transfers	Path
CLEAR Rdest	E1	$Rdest \leftarrow ALUres$	ALU = zero out
INC Rdest	E1 E2 E3	$A \leftarrow Rdest$ $B \leftarrow ALUres$ $Rdest \leftarrow ALUres$ ; $C \leftarrow ALUcout$	ALU = zero out ALU=A+B, Cin=1
DEC Rdest	E1 E2 E3	$A \leftarrow Rdest$ $B \leftarrow ALUres$ $Rdest \leftarrow ALUres$ ; $C \leftarrow ALUcout$	ALU = -1 out ALU=A+B, Cin=0
COMP Rdest	E1 E2 E3	$A \leftarrow Rdest$ $B \leftarrow ALUres$ $Rdest \leftarrow ALUres$	ALU = -1 out ALU=A eor B
ASL Rdest	E1 E2	$A \leftarrow Rdest$ $Rdest \leftarrow Shifter$	Shifter (Arithmetic left)
RETURN Rdest	E1 E2	$A \leftarrow Rdest$ $PC \leftarrow Shifter$	Shifter (Unchanged)



### No Register Instructions

Instruction	Cycle	Transfers	Path
SKIP	E1	$PC \leftarrow PC+1$	

The conditional skip instructions (SKIPPOSITIVE, SKIPNEGATIVE) also take just one execution cycle and may increment the PC depending on the arithmetic carry. The NOP instruction doesn't need any execute cycles, and has no associated register transfers.

